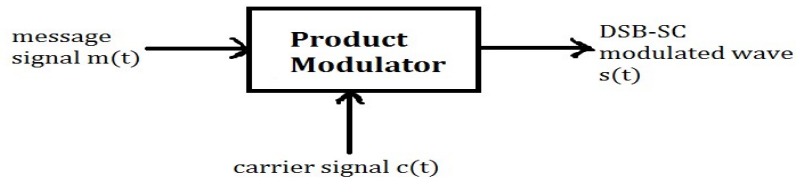


## Lecture 07: DSB-SC Generation

### Generation of DSB-SC


DSB-SC wave is generated by simply multiplying the message signal  $m(t)$  and the carrier signal. Hence the devices used to generate DSB-SC wave are also known Product Modulators.



There are two types of product modulators:

1. Balanced Modulator and
2. Ring Modulator

#### 1. Balanced Modulator:

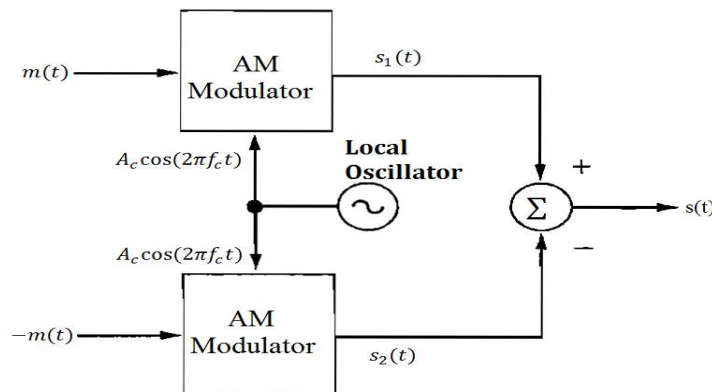

**Fig.1. Block diagram of Balanced Modulator**

It consists of two amplitude modulators that are interconnected in such a way as to suppress the carrier.

One i/p to the amplitude modulator is from an oscillator that generates a carrier wave. The second i/p to the amplitude modulator in the top path is the modulating signal  $m(t)$  while in the bottom path is  $-m(t)$ .

The o/p of two AM modulators are as follows:

$$s_1(t) = A_c[1 + k_a m(t)]\cos(2\pi f_c t) \rightarrow (1)$$

and

$$s_2(t) = A_c[1 - k_a m(t)]\cos(2\pi f_c t) \rightarrow (2)$$

∴ The o/p of the summer is,  $s(t) = s_1(t) - s_2(t)$

$$\Rightarrow s(t) = A_c[1 + k_a m(t)]\cos(2\pi f_c t) - A_c[1 - k_a m(t)]\cos(2\pi f_c t)$$

$$\Rightarrow s(t) = A_c \cos(2\pi f_c t) + k_a m(t) A_c \cos(2\pi f_c t) - A_c \cos(2\pi f_c t) + k_a m(t) A_c \cos(2\pi f_c t)$$

$$\Rightarrow s(t) = 2k_a A_c m(t) \cos(2\pi f_c t) \rightarrow (3)$$

The balanced modulator o/p is equal to the product of the modulating signal  $m(t)$  & the carrier  $c(t)$  except the scaling factor  $2k_a$ .

Taking Fourier Transform on both sides of equation (3), we get

$$S(f) = k_a A_c [M(f - f_c) + M(f + f_c)] \rightarrow (4)$$

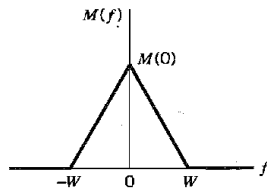


Fig.(a) Message signal Spectrum

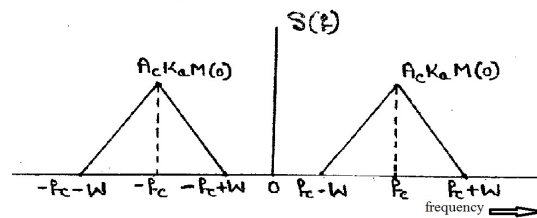


Fig.(b) DSB-SC Spectrum

Since the carrier component is eliminated, the o/p is called DSB-SC signal and its transmission bandwidth is  $2W$  Hz.

## 2. Ring Modulator:

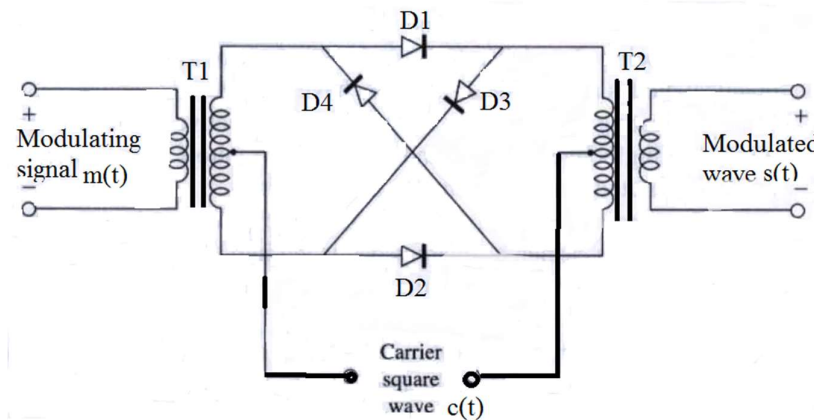


Fig.1. Ring Modulator

Ring modulator is a product modulator used for generating DSB-SC modulated wave. The ring modulator consists of

- i) I/P transformer 'T<sub>1</sub>',
- ii) O/P transformer 'T<sub>2</sub>', and
- iii) Four diodes connected in a bridge circuit (Ring).

The carrier amplitude ' $A_c$ ' is greater than the modulating signal amplitude ' $A_m$ ' i.e.  $A_c > A_m$  and the carrier frequency ' $f_c$ ' is greater than the modulating signal frequency ' $f_m$ ' ( $=W$ ) i.e.  $f_c > W$ , to ensure the diode operation is controlled by  $c(t)$  only.

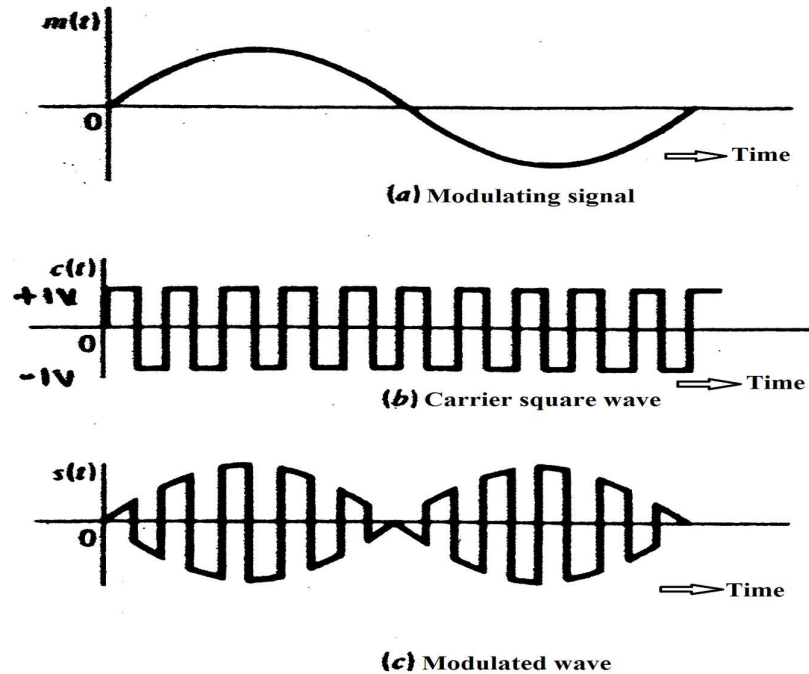


Fig.2. Waveforms in the operation of ring modulator

The diodes are controlled by a carrier square wave  $c(t)$  of frequency ' $f_c$ ' which is applied by means of two centre-tapped transformers.

The modulating signal  $m(t)$  is applied to the primary of i/p RF transformer ' $T_1$ '. The o/p appears across the secondary of the AF transformer ' $T_2$ '.

#### Operation:

- i) When the carrier is positive, the diodes  $D_1$  &  $D_2$  are forward-biased and diodes  $D_3$  &  $D_4$  are reverse biased. Hence the modulator multiplies the message signal  $m(t)$  by  $+1$  (the maximum value of  $|c(t)|$ ) i.e.  $V_o(t) = c(t)m(t) = +m(t)$ .
- ii) When the carrier is negative, the diodes  $D_1$  &  $D_2$  are reverse-biased and diodes  $D_3$  &  $D_4$  are forward-biased. Hence the modulator multiplies the message signal  $m(t)$  by  $-1$  (the negative maximum value of  $|c(t)|$ ) i.e.  $V_o(t) = c(t)m(t) = -m(t)$ .

The carrier square wave  $c(t)$  can be represented by a Fourier series as:

$$c(t) = \frac{4}{\pi} \sum_{n=1}^{\infty} \left( \frac{(-1)^{n-1}}{2n-1} \cos[2\pi f_c (2n-1)t] \right) \rightarrow (1)$$

$$\Rightarrow c(t) = \frac{4}{\pi} \left[ \cos(2\pi f_c t) - \frac{1}{3} \cos(6\pi f_c t) + \dots \right] \rightarrow (2)$$

The ring modulator output is  $s(t) = c(t) \cdot m(t) \rightarrow (3)$

Substituting equation (2) in equation (3), we get

$$s(t) = \frac{4}{\pi} \left[ \cos(2\pi f_c t) - \frac{1}{3} \cos(6\pi f_c t) + \dots \right] \cdot m(t)$$

$$\Rightarrow s(t) = \frac{4}{\pi} m(t) \cos(2\pi f_c t) - \frac{4}{3\pi} m(t) \cos(6\pi f_c t) + \dots \rightarrow (4)$$

Taking Fourier transform on both sides of equation (4), we get

$$S(f) = \frac{4}{2\pi} [M(f - f_c) + M(f + f_c)] - \frac{4}{6\pi} [M(f - 3f_c) + M(f + 3f_c)]$$

$$\Rightarrow S(f) = \frac{2}{\pi} [M(f - f_c) + M(f + f_c)] - \frac{2}{3\pi} [M(f - 3f_c) + M(f + 3f_c)] \rightarrow (5)$$

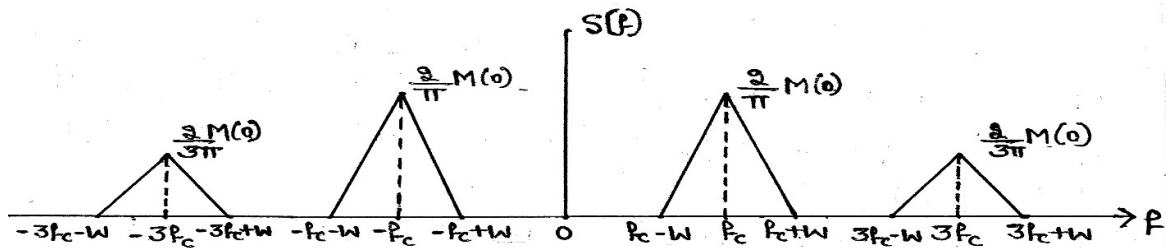


Fig.3. Amplitude spectrum of S(f)

The DSB-SC wave is extracted from  $s(t)$  by passing equation (4) through an ideal BPF having centre frequency  $f_c$  and bandwidth equal to  $2W$  Hz.

The O/P of the BPF is

$$s(t) = \frac{4}{\pi} m(t) \cos(2\pi f_c t).$$